

## Introduction to Logic Design

CSci 2021: Machine Architecture and Organization  
Lecture #18, March 4th, 2015

Your instructor: Stephen McCamant

Based on slides originally by:  
Randy Bryant, Dave O'Hallaron, Antonia Zhai

- 1 -

## Overview of Logic Design

### Fundamental Hardware Requirements


- Communication
  - How to get values from one place to another
- Computation
- Storage

### Bits are Our Friends

- Everything expressed in terms of values 0 and 1
- Communication
  - Low or high voltage on wire
- Computation
  - Compute Boolean functions
- Storage
  - Store bits of information

- 2 -


## Digital Signals

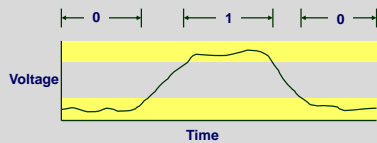


- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
  - Either high range (1) or low range (0)
  - With guard range between them
- Not strongly affected by noise or low quality circuit elements
  - Can make circuits simple, small, and fast

- 3 -

## Computing with Logic Gates

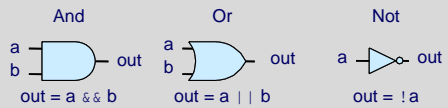


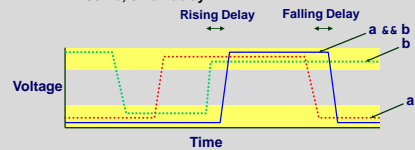- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
  - With some, small delay



- 4 -

## Combinational Circuits

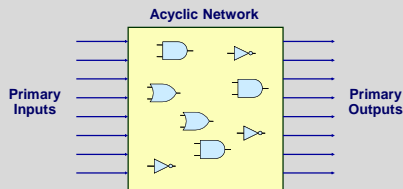


### Acyclic Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

- 5 -

## Bit Equality

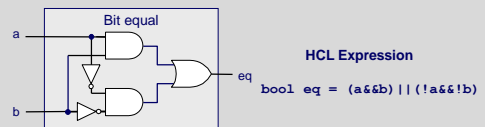


- Generate 1 if a and b are equal

### Hardware Control Language (HCL)

- Very simple hardware description language
  - Boolean operations have syntax similar to C logical operations
- We'll use it to describe control logic for processors


- 6 -

## Word Equality

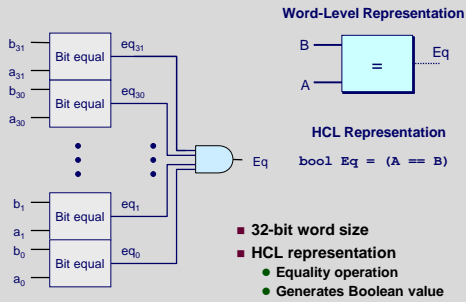

- 7 -


## Bit-Level Multiplexor

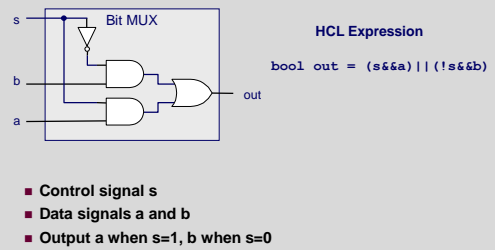

- 8 -

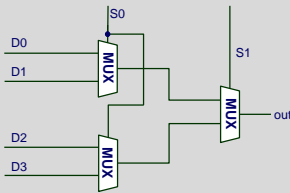
## Exercise Break: 4-input Mux

- Suppose we want to choose between 4 signals, D0, D1, D2, and D3, using two selector bits S0 and S1
- Can you build this out of 2-input muxes?



- 9 -


## Word Multiplexor

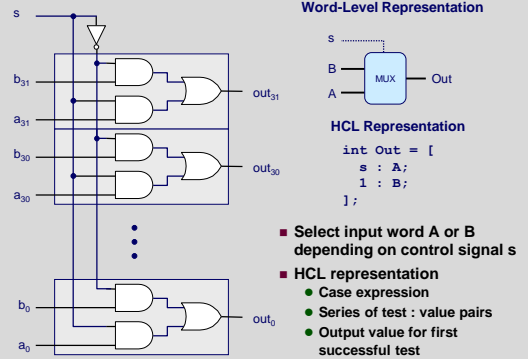


- 10 -

## HCL Word-Level Examples

### Minimum of 3 Words

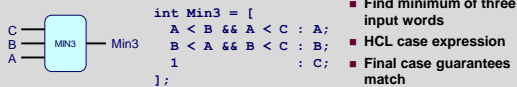


### 4-Way Multiplexor

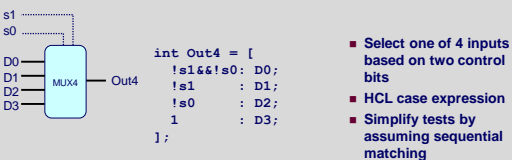

- 11 -


## Arithmetic Logic Unit

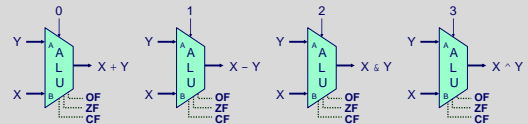

- Combinational logic
  - Continuously responding to inputs
- Control signal selects function computed
  - Corresponding to 4 arithmetic/logical operations in Y86
- Also computes values for condition codes

- 12 -

## Registers

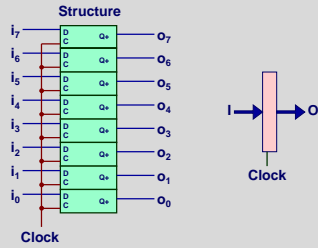

- Stores word of data
  - Different from *program registers* seen in assembly code
- Collection of edge-triggered latches
- Loads input on rising edge of clock

- 13 -


## Register Operation




- Stores data bits
- For most of time acts as barrier between input and output
- As clock rises, loads input

- 14 -

## State Machine Example

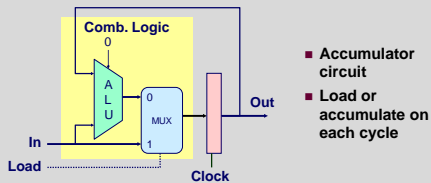


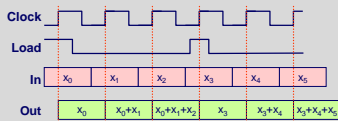- Accumulator circuit
- Load or accumulate on each cycle



- 15 -


## Random-Access Memory

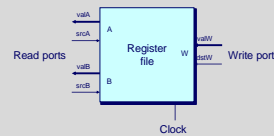

- Stores multiple words of memory
  - Address input specifies which word to read or write
- Register file
  - Holds values of program registers
  - `%eax, %esp, etc.`
  - Register identifier serves as address
    - » ID 15 (0xF) implies no read or write performed
- Multiple Ports
  - Can read and/or write multiple words in one cycle
    - » Each has separate address and data input/output

- 16 -

## Register File Timing

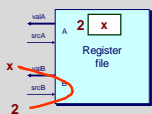


### Reading

- Like combinational logic
- Output data generated based on input address
  - After some delay
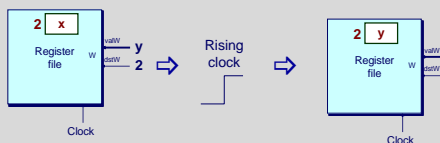
### Writing

- Like register
- Update only as clock rises



- 17 -

## Hardware Control Language

- Very simple hardware description language
- Can only express limited aspects of hardware operation
  - Parts we want to explore and modify

### Data Types

- `bool`: Boolean
  - `a, b, c, ...`
- `int`: words
  - `A, B, C, ...`
  - Does not specify word size—bytes, 32-bit words, ...

### Statements

- `bool a = bool-expr ;`
- `int A = int-expr ;`

- 18 -

## HCL Operations

- Classify by type of value returned

### Boolean Expressions

- Logic Operations
  - $a \ \&\& \ b, a \ || \ b, !a$
- Word Comparisons
  - $A == B, A != B, A < B, A <= B, A >= B, A > B$
- Set Membership
  - $A \ \text{in} \ \{ B, C, D \}$ 
    - » Same as  $A == B \ || \ A == C \ || \ A == D$

### Word Expressions

- Case expressions
  - $[ a : A; b : B; c : C ]$
  - Evaluate test expressions  $a, b, c, \dots$  in sequence
  - Return word expression  $A, B, C, \dots$  for first successful test

- 19 -

## Summary

### Computation

- Performed by combinational logic
- Computes Boolean functions
- Continuously reacts to input changes

### Storage

- Registers
  - Hold single words
  - Loaded as clock rises
- Random-access memories
  - Hold multiple words
  - Possible multiple read or write ports
  - Read word when address input changes
  - Write word as clock rises

- 20 -