

Logic Design V

CSci 2021: Machine Architecture and Organization
Lecture #40, May 4th, 2015

Your instructor: Stephen McCamant

1


Timing for Flip-Flops

- **Input must be steady around clock edge for reliable operation**
 - Setup time: amount of time before clock input must be right
 - Hold time: amount of time after clock that input must right
- **Delay before output changes**
 - Clock-to-output time: delay between clock edge and output edge
- **Important fact:**
 - (hold time) < (clock-to-output time)
 - If true of two flip-flops, it is safe to connect output of one to input of another, on the same clock

2

Metastability


■ Analogy:

 

- **Flip-flop tries to return to a stable state**
 - Self-correcting feedback
- **But, if close to metastable point:**
 - Might take a long time to "decide"
 - Must avoid this situation for a reliable circuit

3

Shift Register

 

- **Flip-flops connected in series**
- **Behavior:**
 - Sequence of bits each move one stage per clock cycle
- **Variations:**
 - Serial or parallel input
 - Series or parallel output
 - Shift only one some cycles

4

Counters

- **Simple kind of time-varying digital system**
 - Produces a single sequence of states, repeating
 - Changes every cycle or on a count pulse
- **Example: 3-bit binary up-counter**
 - Produces 000, 001, 010, 011, 100, 101, 110, 111, 000, 001, ...
- **Variations:**
 - Down-counters
 - Decade counters (for decimal): 0 through 9
 - Gray code: sequence where only one bit changes at a time
 - Ring counter: circular shift register producing one-hot outputs

5


State Machines

- **State machine perspective:**
 - If a device has limited memory, we can enumerate its possible states
 - n bits of memory \rightarrow at most 2^n states
 - Inputs cause state transitions
 - Outputs depend on state and possibly inputs
- **General approach for designing sequential circuits**
 - Enumerate states
 - Determine state transitions and I/O
 - Last two summarized in *state transition diagram*
 - Use flip-flops to remember state
 - Use combinational logic to implement update and output functions

6


Counters as State Machines

 - **Simplified special case**
 - Output is generally identical to state
 - No input other than a clock
 - State transition diagram is a single cycle
- **Three-bit up counter:**



7

Counter Block Diagram

 

- **Register: parallel D flip-flops**
- **State update is a combinational circuit**
 - For 3-bit up counter, increment mod 8

8

Administrative Notes

- **Final exam: Thursday, May 14th**
 - Location: 133 Tate Physics, same as regular lectures
 - Time: 8:00am-10:00am, same rules as quizzes
 - Topic coverage: comprehensive, but extra weight on post-quiz-2 material
- **Assignment V due Friday in lecture**
- **Wednesday and Friday lecture topics: review**
 - Wednesday: outline of course topics, course evaluations
 - Bring pen or pencil
 - Friday: practice problems from VM through logic design
- **Prof. Zhai will substitute for me on Friday and the final**
 - Still have office hours next week


9

Running Example: Vending Machine

- **Sell some 30-cent product**
 - 3 oz cans of soda, etc.
- **Inputs: coin detectors**
 - Nickels (5 cents), dimes (10 cents), quarters (25 cents)
- **Output: can dispenser**
- **State: amount of money received so far**

10


State Diagram: Starting

 

- **Think about all possible sequences of inputs**
- **States are the same if future behavior is the same**
 - E.g., Two nickels equivalent to one dime

11

State Diagram: Up To \$0.30

 

- **Check: are there N, D, and Q edges out of every state?**

12


Vending Machine Design

What to do about overpayment?

1. Just keep the money
 2. Apply to the next transaction
 3. Reject a single coin
 4. Abort the whole transaction
 5. Make change
- } Can do with current I/O
} Require new actions
} Many complications

13


Overpayment State Diagram

 

- What can we do with this edge?

14

Overpayment Choices

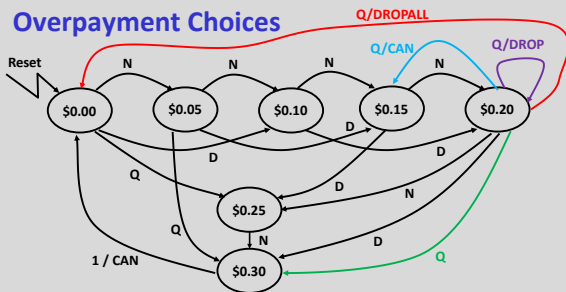

1. Just keep the money
2. Apply to the next transaction
3. Reject a single coin
4. Abort the whole transaction

15

Two Ways to Handle Output

Moore machine


- Output depends only on the current state
- Output changes only with the clock
- Output written in the state circle
- Requires more states

Mealy machine

- Output based on state and inputs
- Output can change asynchronously
- Output written with transition, after a slash
- Requires fewer states


16

Moore Machine Block Diagram

 

17

Mealy Machine Block Diagram

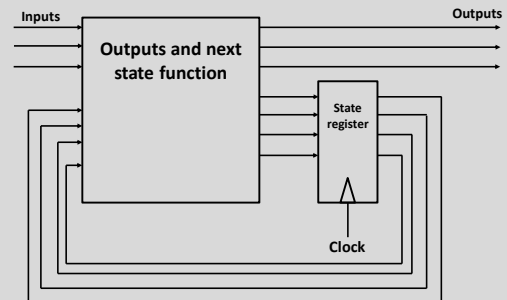

18

State Diagram Conventions

- **Indicate the starting/reset state**
 - With an arrow coming from nowhere
- **Input signals on edges can be separated with commas**
 - D, Q: dime or quarter
- **Or, input signals can be combinational functions**
 - D | Q: same
- **Edges leaving a state must be mutually exclusive**
 - "Deterministic" state machine
- **Often omitted:**
 - Transitions that stay in the same state
 - Especially if all inputs inactive
 - Inactive outputs

19

Choosing a State Encoding

- **Unique pattern of state bits for each state**
 1. One-hot
 - Simplifies logic if not too many states
 - Scales poorly with many states
 2. Binary encoding
 - Fewer wires and flip-flops
 - Logic may be more complicated
- **Careful choice of encoding makes logic simpler**
 - Use similar bit patterns for similar states
 - There are automated CAD tools for this too

20

State Machine Logic

- **Given encoding, create truth tables**
- **Then, reduces to combinational design**
 - Karnaugh maps, etc.
- **Optionally, could use other kinds of flip-flops**
 - Sometimes leads to modest simplification


21

Some Implementation Technologies

- **Breadboard and SSI ICs**
 - E.g., "hex inverter" chip
 - For production, design a printed circuit board
 - 70s technology, good for hobby projects and intro courses
- **Application-Specific Integrated Circuit (ASIC)**
 - I.e., rent a microchip factory, like Intel's
 - Cost effective only in large quantities
- **Reconfigurable logic**
 - "Field-Programmable Gate Array" (FPGA)
 - General-purpose hardware can be electronically configured into a chosen circuit
 - Blurs the line between software and hardware

22

FPGA Overall Structure

 

23

Configurable Logic Block (CLB)

- **A small unit of reconfigurable hardware**
- **Might contain, for instance:**
 - An arbitrary 5-input Boolean function implemented as a lookup table
 - A full adder
 - A D flip-flop
- **The lookup table is just an SRAM**
 - So it's programmable
 - But in operation, it typically stays fixed after bootup

24

Interconnect

- **Have to wire these blocks into a circuit**
- **CLBs are connected with configurable channels**
 - I.e., wires with transistor-based switches at intersections
- **Statically configured**
 - A certain wire is always used for the same connection
 - Switches increase delay compared to a plain wire
- **Length tradeoffs**
 - Adjacent blocks have fastest connections
 - Many switches → optimized for short paths
 - Smaller number of long wires
 - Specialized lines for clock distribution

25

Programming and Using FPGAs

- **Automatic computerized layout standard**
 - Proprietary tools optimized by FPGA manufacturers
- **Program might be:**
 - Loaded at power-on
 - Stored in on-FPGA flash memory
- **What are FPGAs good for?**
 - Prototyping complex hardware descriptions
 - Low- to medium-volume specialized devices
 - Accelerating certain very-parallel computations

26